

**2022/TDC (CBCS)/EVEN/SEM/
PHSHCC-403T/115**

TDC (CBCS) Even Semester Exam., 2022

PHYSICS

(Honours)

(4th Semester)

Course No. : PSHHCC-403T

(Analog System and Applications)

Full Marks : 50

Pass Marks : 20

Time : 3 hours

*The figures in the margin indicate full marks
for the questions*

SECTION—A

Answer any ten of the following questions : $2 \times 10 = 20$

- 1. What do you mean by *N*- and *P*-type semiconductors?**
- 2. Discuss the barrier formation in *P-N* junction diode.**
- 3. Draw the circuit diagram of centre-tapped full-wave rectifier.**

(2)

4. Distinguish between a Zener diode and an Ordinary *P-N* junction diode.
5. Discuss the principle of operation of light emitting diodes.
6. Draw the DC load line of a transistor. What do you mean by *Q*-point of a biased transistor?
7. Explain the term 'transistor biasing'.
8. Draw the *h*-parameter equivalent circuit of a transistor connected in CE mode.
9. Why is the fixed bias not preferred over a voltage divider bias? Explain.
10. What do you mean by feedback in amplifiers? Explain.
11. Discuss about the Barkhausen's criterion for self-sustained oscillations.
12. Draw the circuit diagram of a Hartley oscillator.
13. Write the difference between an ideal and practical Op-Amp.

(3)

14. Define CMRR and slow rate of an OP-Amp.
15. Draw the block diagram of IC-741.

SECTION—B

Answer any *five* of the following questions : $6 \times 5 = 30$

16. What do you mean by d.c. and a.c. resistance of a *P-N* junction diode? Discuss the *V-I* characteristic curve of a *P-N* junction diode.
2+4=6
17. Obtain the expression for ripple factor and rectification efficiency of a full-wave rectifier. 6
18. Draw the circuit diagram of a transistor in CE mode and then obtain the expression for current gain.
2+4=6
19. What do you mean by a Zener diode? With proper circuit diagram, explain its working as a voltage regulator.
2+4=6
20. Discuss the voltage divider bias technique and obtain the expression for its stability factor. 6

(4)

- 21.** Explain the working of a CE transistor amplifier. Obtain the expression for its voltage gain and power gain. 2+4=6
- 22.** Draw the circuit diagram of a two-stage RC-coupled amplifier and explain its frequency response curve. 2+4=6
- 23.** Explain the working of an RC-phase shift oscillator and obtain the expression for its frequency of oscillations. 6
- 24.** What do you mean by Open-loop and Closed-loop gain of an OP-Amp? Obtain the expression for closed-loop gain of an inverting amplifier using Op-Amp. 2+4=6
- 25.** Write short notes on the following : 3+3=6
- (a) Adder
- (b) Integrator
- using OP-Amps
